



Information Technology Institute (ITI)

CMOS ANALOG IC DESIGN

LAB 1

ALHUSSEIN GAMAL


Table of contents:

Content	Page
Low Pass Filter	3
• Transient Analysis	3
• AC Analysis	8
MOSFET Characteristics	13
• ID vs VGS	13
• gm vs VGS	17
• ID vs VDS	18
• gm and ro in triode region	19

PART 1: LOW PASS FILTER SIMULATION (LPF)

1. Transient Analysis


1) The circuit schematic is shown.

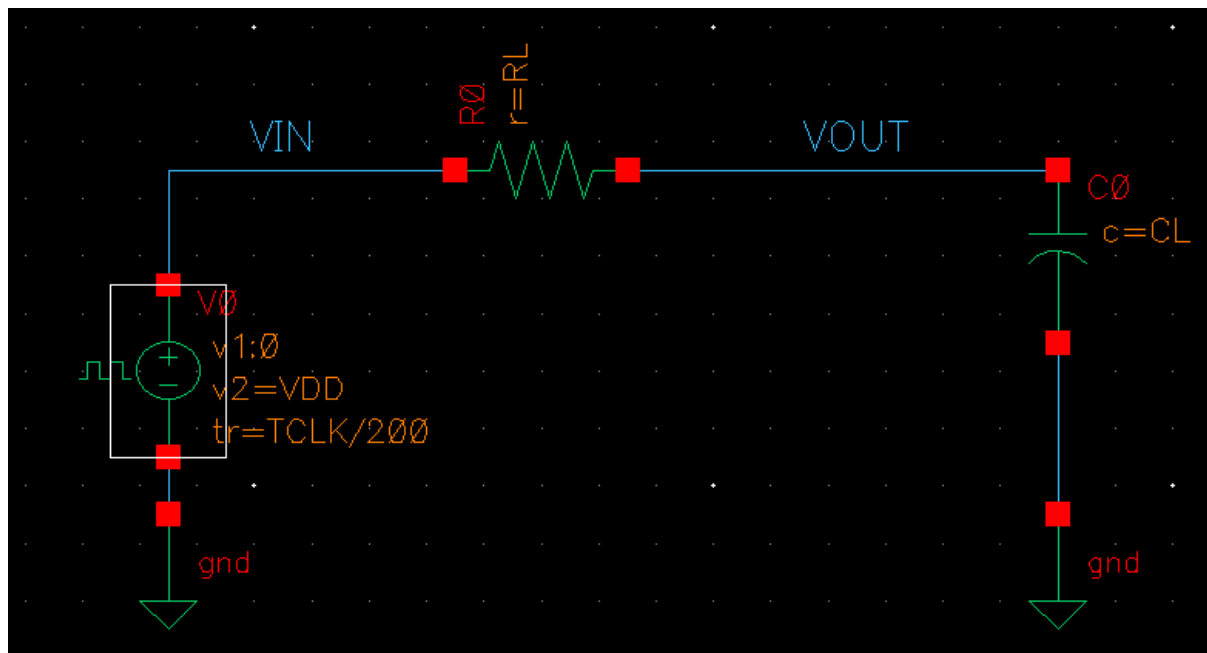

2) Parameters of the square pulse input signal are shown.

Voltage 1	0 V
Voltage 2	VDD V
Period	TCLK s
Delay time	TCLK/4 s
Rise time	TCLK/200 s
Fall time	TCLK/200 s
Pulse width	TCLK/2 s

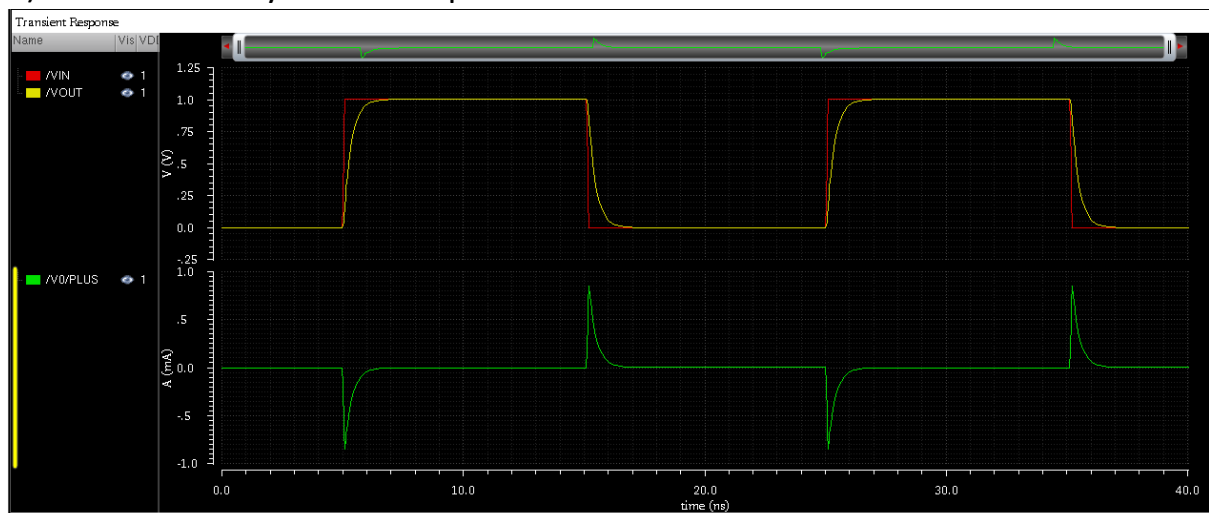3) Transient Analysis for two periods is shown



4)

Rise time

`riseTime(VT("/VOUT") 0 nil 1 nil 10 90 nil "time")` Calculator Expression

riseTime(VT("/VOUT") 0 nil 1 nil 10...	
VDD	riseTime..."time")
1 1.000	663.0E-12

Tabular Result

Fall Time

`fallTime(VT("/VOUT") 1 nil 0 nil 90 10 nil "time")` Calculator Expression

fallTime(VT("/VOUT") 1 nil 0 nil 90 ...	
VDD	fallTime..."time")
1 1.000	663.0E-12

Tabular Result

5) Comparison between the Results.

analytical results calculations:

The proportionality constant can be derived from the knowledge of the step response of the network to a unit step function input signal of V_0 amplitude:

$$V(t) = V(O)(1 - e^{-t/\tau})$$

solving the equation ==> we get $t = -\tau \ln(1 - V(t)/V(O))$

At t_1 and t_2 ==> 10% of VDD and 90% Of VDD

$$V(t_1)/V(O) = 0,1 \quad \&\& \quad V(t_2)/V(O) = 0,9$$

$$t = -\tau \ln(1 - 0,1) = -\tau \ln(9/10) = \tau \ln(10/9) = 2.197 * \tau$$

$$t_{\text{rise}} = 2.197 * 0.3 \text{ ns} = 0.6591 \text{ ns}$$

$$t_{\text{fall}} = -2.197 * 0.3 \text{ ns} = |-0.6591| = 0.6591 \text{ ns}$$


Analytical	Simulation
Rise time : 0.6591 ns	Rise Time : 0.6630 ns
Fall time : 0.6591 ns	Fall time : 0.6630 ns

6) Parametric Sweep for $R = 1K : 1K : 5K$

For different values of R, Results are shown below:

Point	Test	Output	Nominal	Spec	Weight	Pass/Fail
Parameters: RL=1k						
1	lab1:lpf:1	VIN				
1	lab1:lpf:1	VOUT				
1	lab1:lpf:1	I				
1	lab1:lpf:1	trise	663p			
1	lab1:lpf:1	tfall	663p			
Parameters: RL=2k						
2	lab1:lpf:1	VIN				
2	lab1:lpf:1	VOUT				
2	lab1:lpf:1	I				
2	lab1:lpf:1	trise	1.311n			
2	lab1:lpf:1	tfall	1.311n			
Parameters: RL=3k						
3	lab1:lpf:1	VIN				
3	lab1:lpf:1	VOUT				
3	lab1:lpf:1	I				
3	lab1:lpf:1	trise	1.974n			
3	lab1:lpf:1	tfall	1.974n			
Parameters: RL=4k						
4	lab1:lpf:1	VIN				
4	lab1:lpf:1	VOUT				
4	lab1:lpf:1	I				
4	lab1:lpf:1	trise	2.633n			
4	lab1:lpf:1	tfall	2.633n			
Parameters: RL=5k						
5	lab1:lpf:1	VIN				
5	lab1:lpf:1	VOUT				
5	lab1:lpf:1	I				
5	lab1:lpf:1	trise	3.293n			
5	lab1:lpf:1	tfall	3.293n			

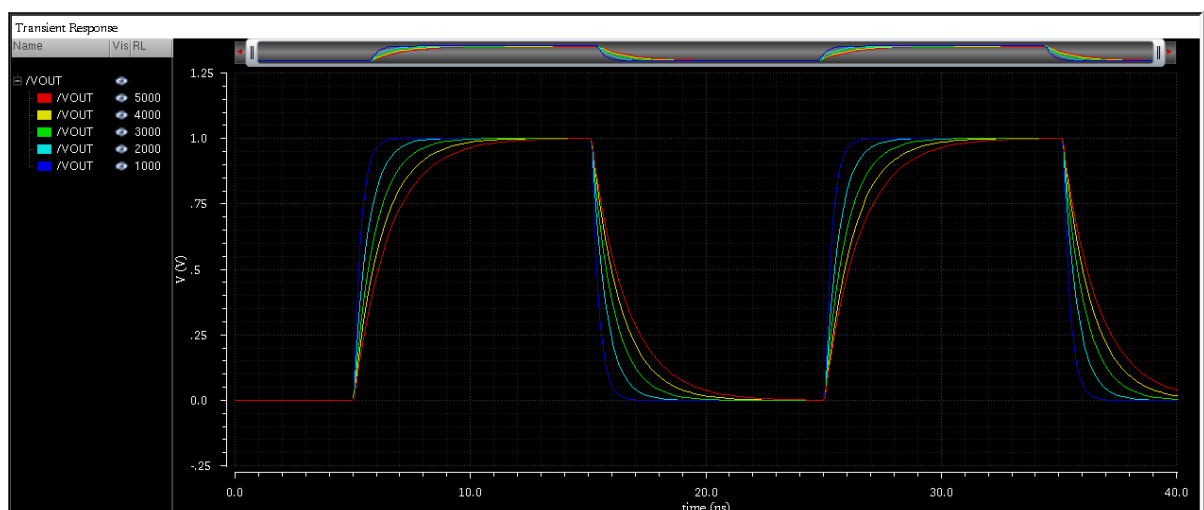
Plot of Vout vs time (on using a parametric sweep on R)




The graph affirms our knowledge that the higher the value of R, the more time it takes to charge the capacitor, and also the less time it takes for the capacitor to discharge. This is illustrated on the graph; As R increases, Vout graph gets

less steep while charging (slower charging) and gets less steep while discharging (slower discharging).

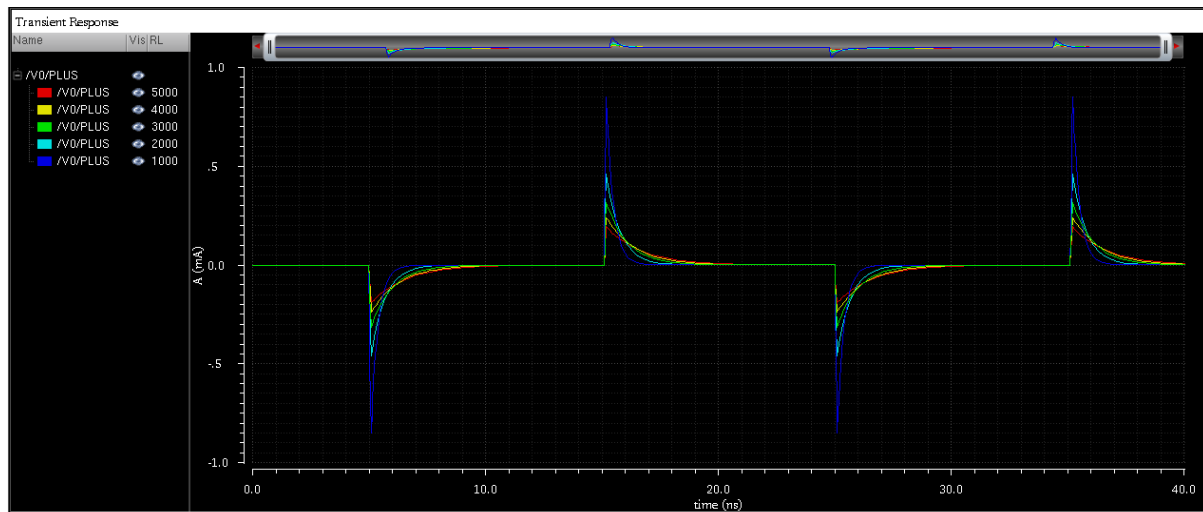Current vs time (on using a parametric sweep on R)



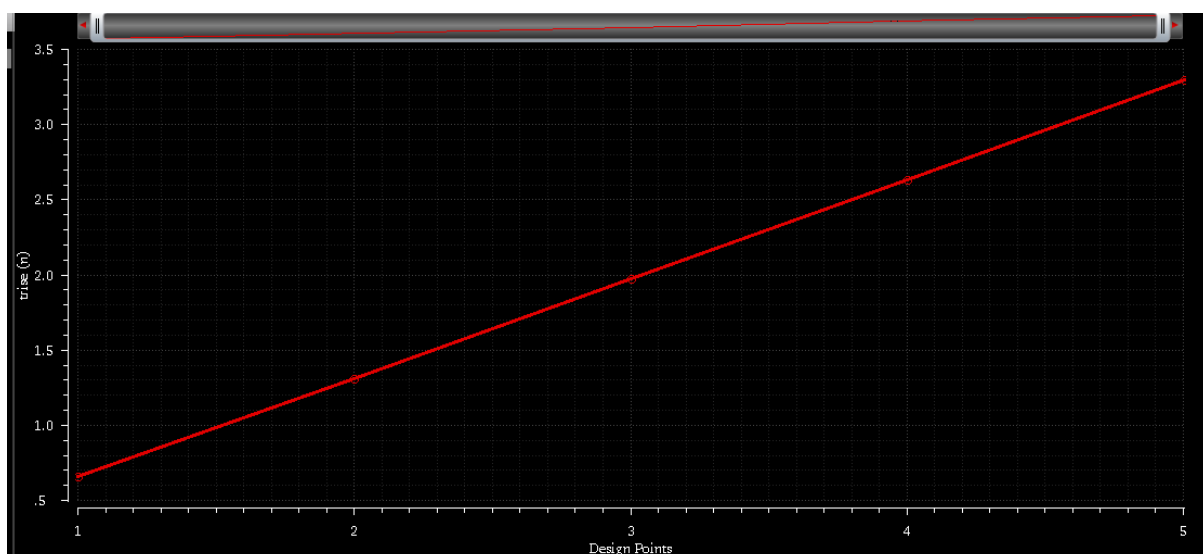Rise and Fall times across the parametric sweep




The rise and fall times are equal, as we expect for a first-order system.

The rise and fall times increase across design points; They increase as we increase R.


2. AC Analysis

1) Bode Plot Results


Magnitude

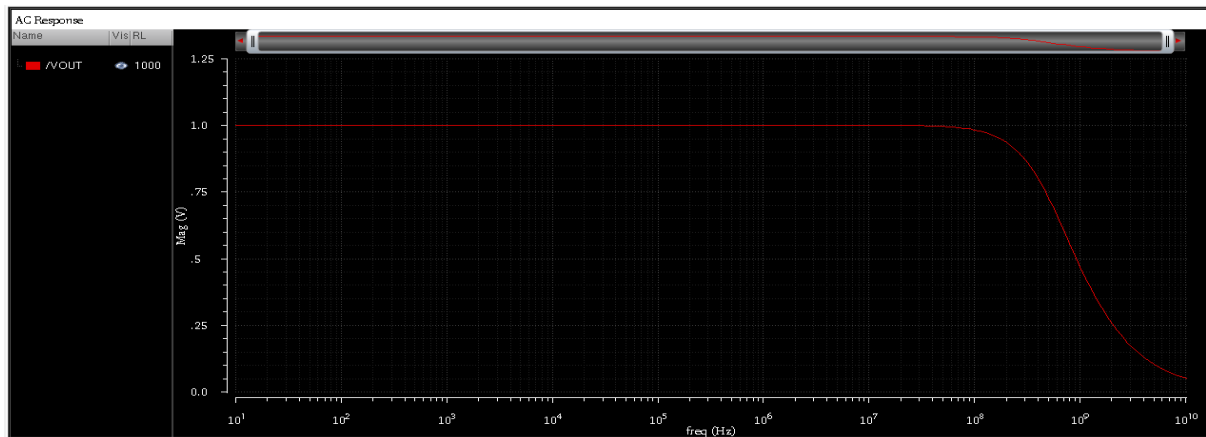

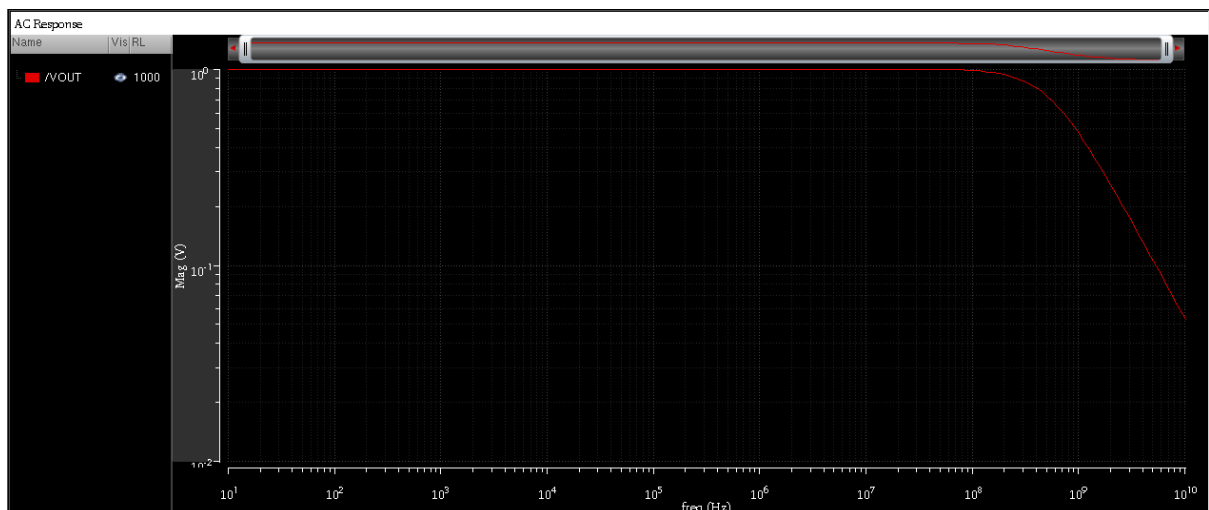On log scale, we get the shown result for the magnitude of V_{out}




Phase

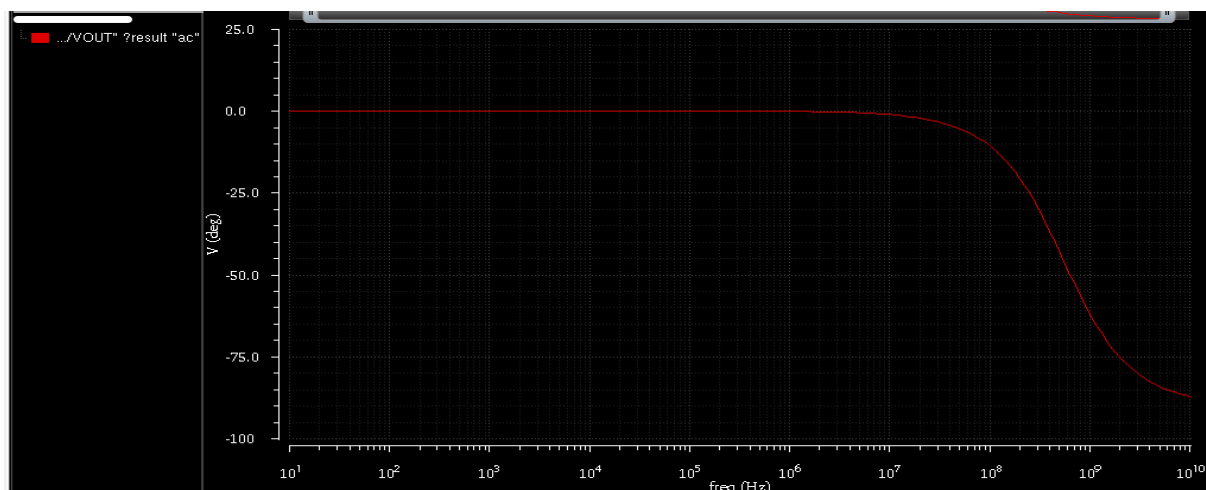

2) DC gain and Bandwidth

dB20 graph

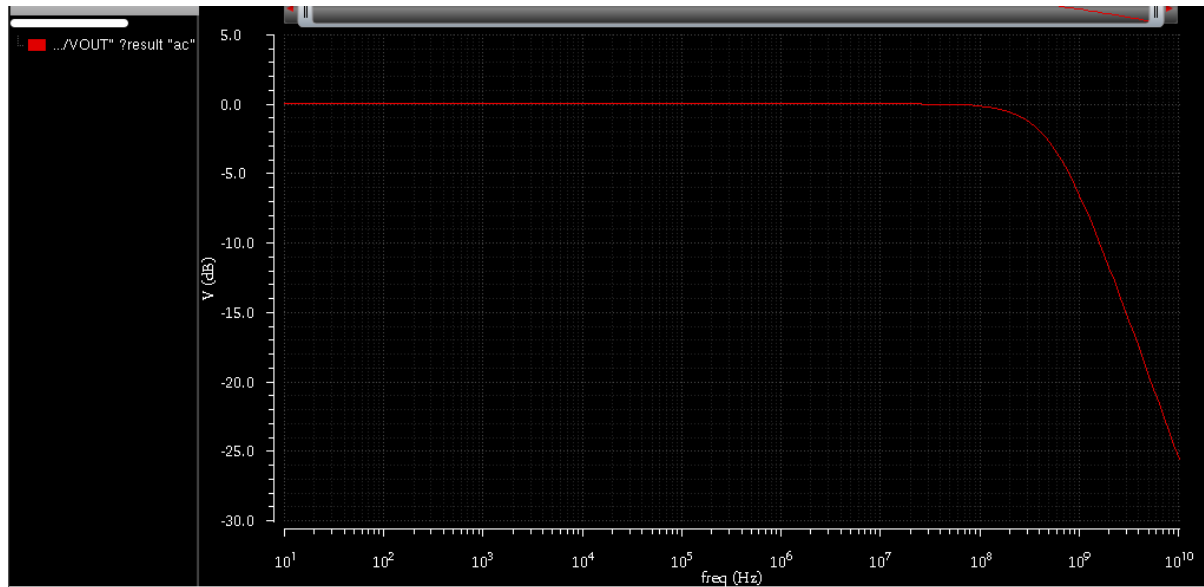

DC gain and 3dB Bandwidth values are shown

Test	Output	Nominal	Spec	Weight	Pass/Fail
lab1:lpf:1	VIN				
lab1:lpf:1	VOUT				
lab1:lpf:1	I				
lab1:lpf:1	3dB	529.7M			
lab1:lpf:1	DC gain	1			

3) Results Comparison

	analytical results calculations:
	given $R = 1 \text{ k ohms}$ && $C=0.3 \text{ p F}$
	$\text{Bandwidth} = 1/(2 \cdot \pi \cdot C \cdot R) \Rightarrow \text{Bandwidth} = 530.516477 \text{ M HZ}$
	Gain as there is no load at the output voltage and Gain equations is
	$\text{Gain} = 1+R2/R1 \text{ \&\& } R2/R1 =0 \text{ Gain} = 1$

Analytical	Simulation
Bandwidth : 530.516477 MHZ	Bandwidth : 529.7 MHZ
Gain = 1	Gain = 1

4)


Point	Test	Output	Nominal	Spec	Weight	Pass/Fail
Parameters: RL=1k						
1	lab1:lpf:1	VIN				
1	lab1:lpf:1	VOUT				
1	lab1:lpf:1	I				
1	lab1:lpf:1	DC gain	1			
1	lab1:lpf:1	3dB BW	529.7M			
Parameters: RL=10k						
2	lab1:lpf:1	VIN				
2	lab1:lpf:1	VOUT				
2	lab1:lpf:1	I				
2	lab1:lpf:1	DC gain	1			
2	lab1:lpf:1	3dB BW	52.97M			
Parameters: RL=100k						
3	lab1:lpf:1	VIN				
3	lab1:lpf:1	VOUT				
3	lab1:lpf:1	I				
3	lab1:lpf:1	DC gain	1			
3	lab1:lpf:1	3dB BW	5.297M			
Parameters: RL=1M						
4	lab1:lpf:1	VIN				
4	lab1:lpf:1	VOUT				
4	lab1:lpf:1	I				
4	lab1:lpf:1	DC gain	1			
4	lab1:lpf:1	3dB BW	529.7k			

Results of simulation.


$BW = 1/(2\pi \cdot R \cdot C)$. That is BW is inversely proportional to R. As R increases by a factor of 10, BW decreases by a factor of 10, as can be observed.

Gain is independent of R, so it didn't change.

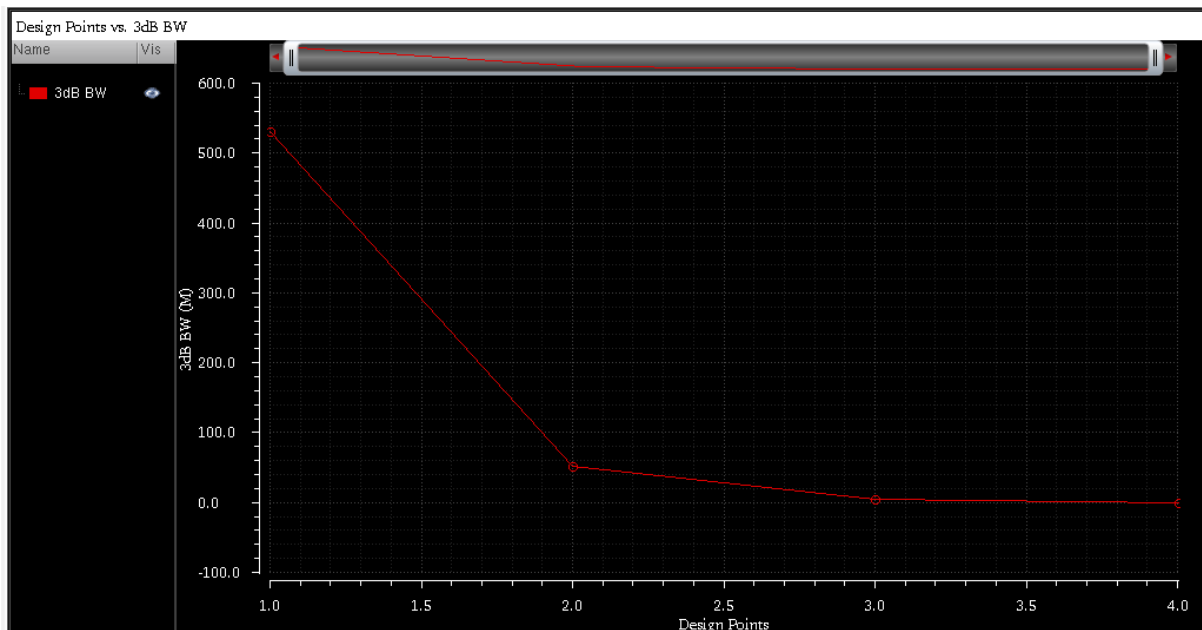
3dB bandwidth across design points (different R values) are shown below.



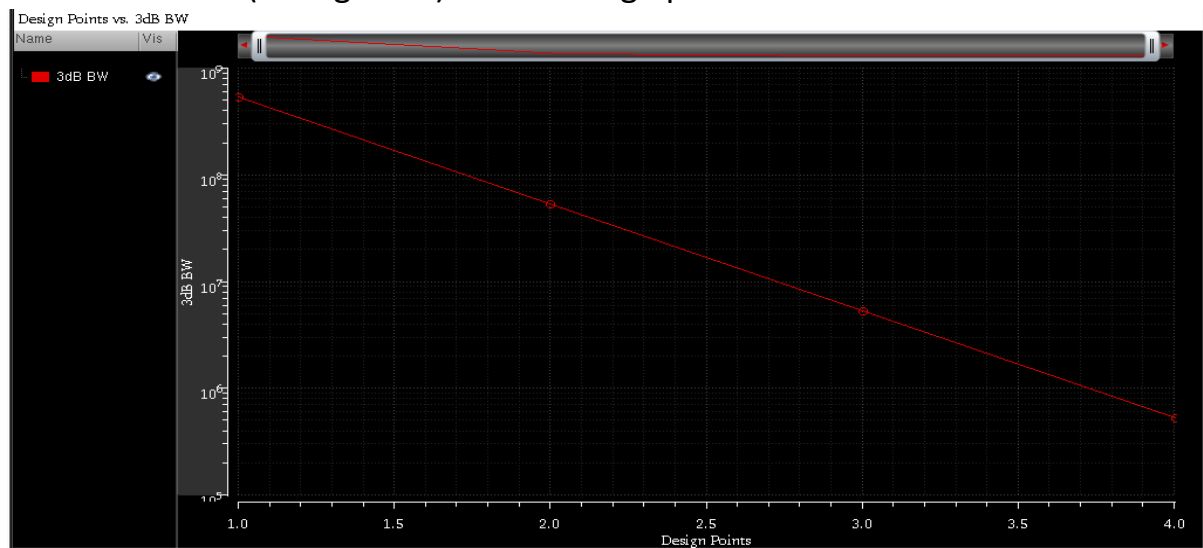
3dB bandwidth (on log scale) across design points



Vout across design points

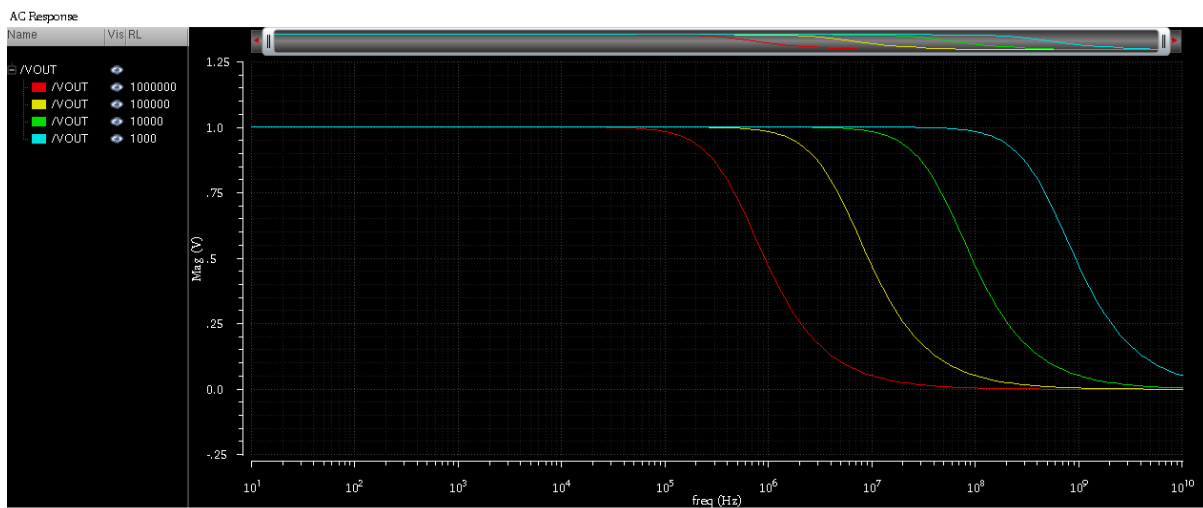


Vout across design points on log scale

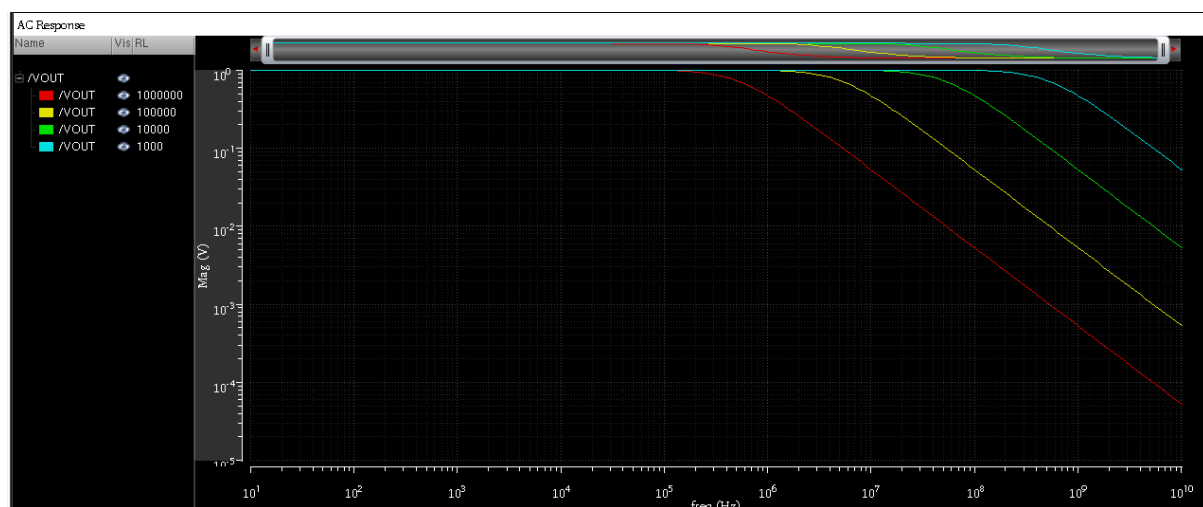

In the above graph, we can observe the bandwidth decreasing as R increases

PART 2: MOSFET CHARACTERISTICS


The circuit schematic is shown

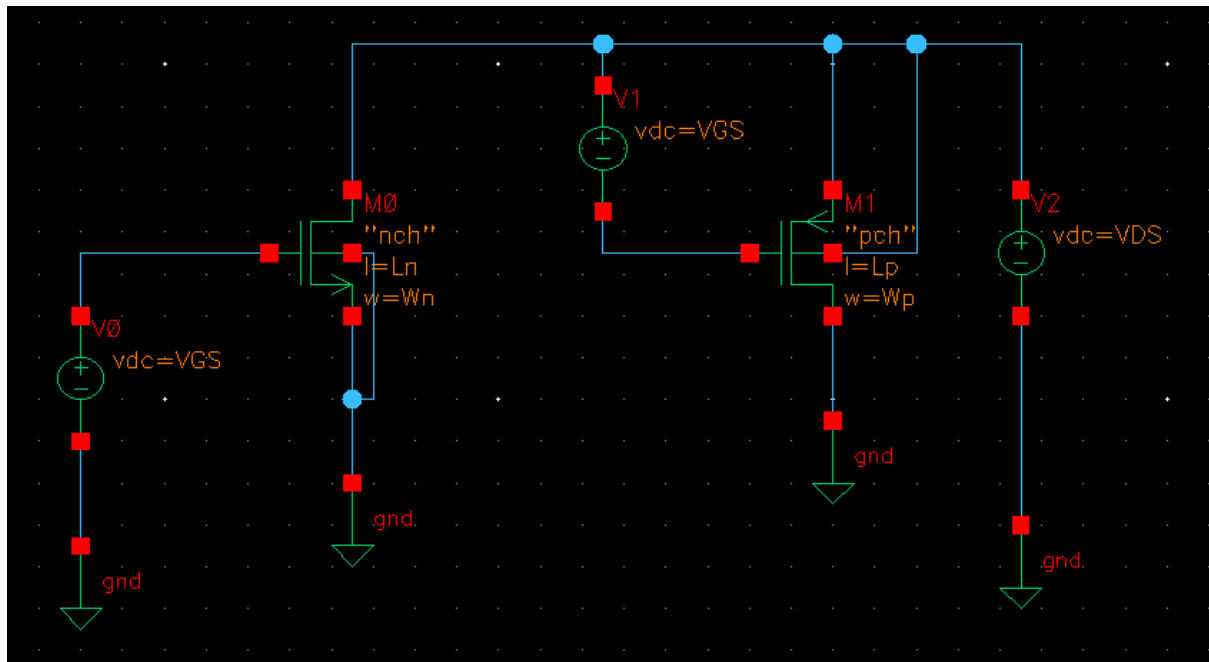

1.ID vs VGS

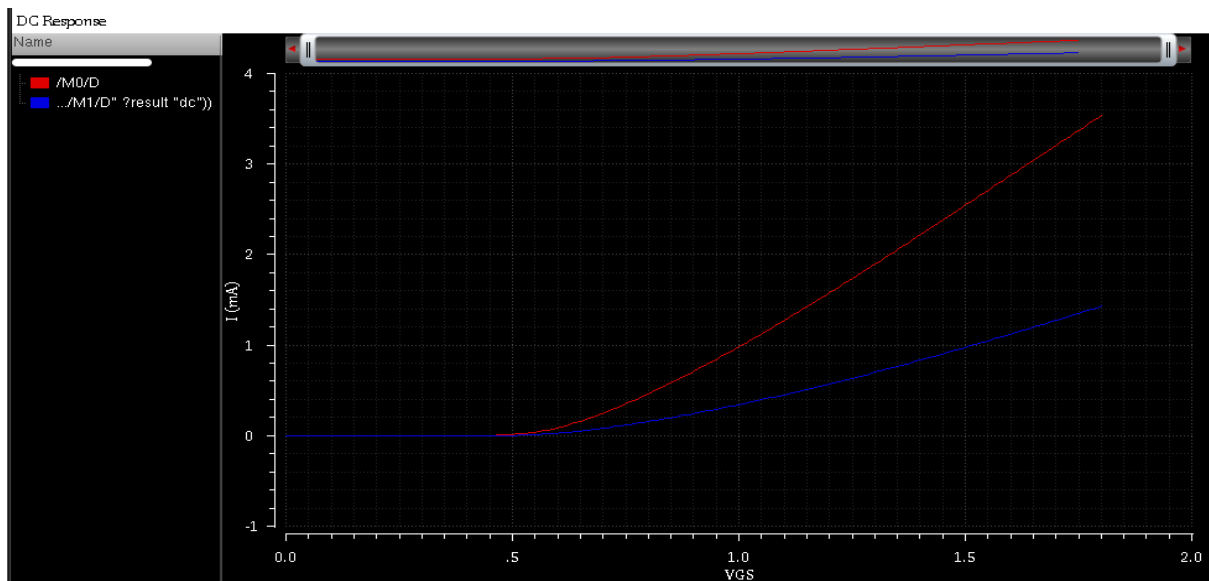
1) Short channel device

ID(NMOS) is shown in red, and the absolute value of ID(PMOS) is shown in blue.




Long channel device

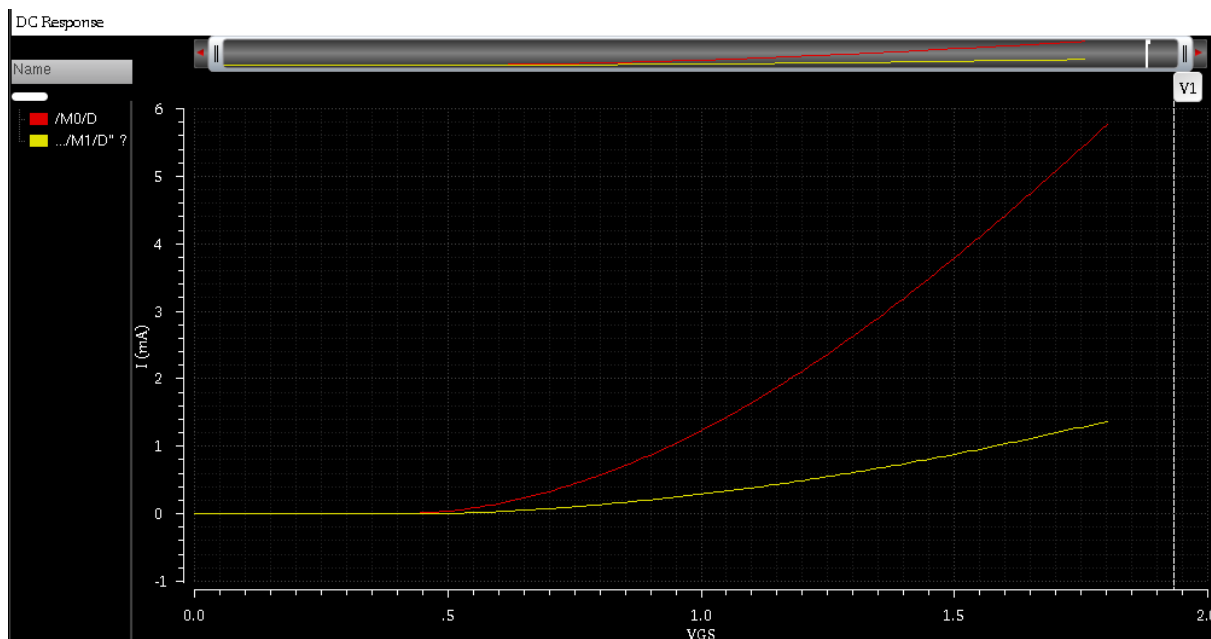$I_D(\text{NMOS})$ is shown in red, and the absolute value of $I_D(\text{PMOS})$ is in blue.




Ideally the two graphs should be the same, but actually there's a slight difference to be noticed if we look carefully.

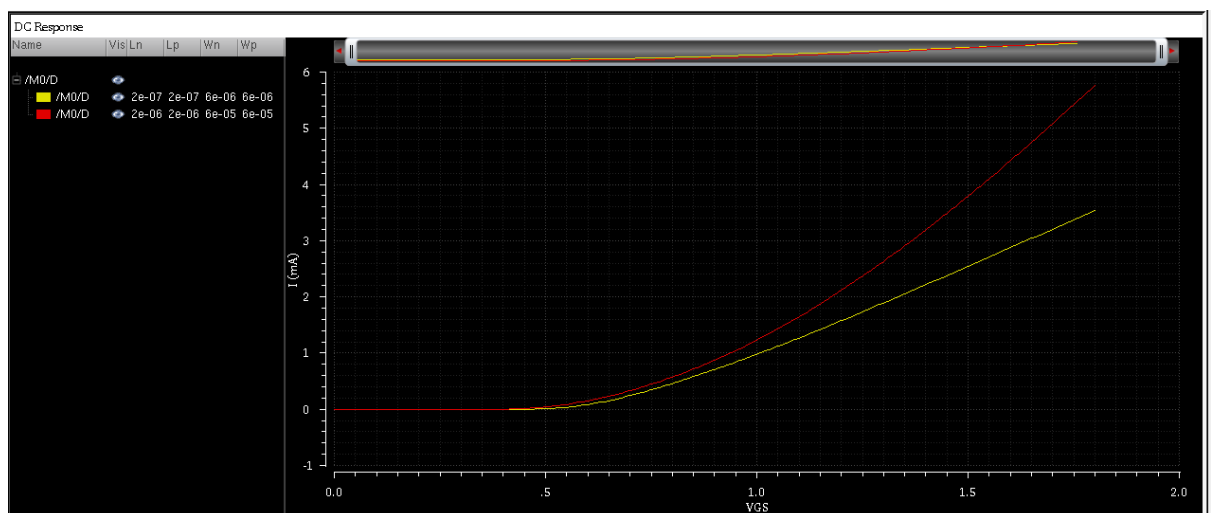2) NMOS: Long Channel (red) vs Short Channel (yellow)



We can observe that the current is higher for the long channel device. The current in the short channel device starts as a quadratic function, but follows a linear trend thereafter due to the short channel effect.

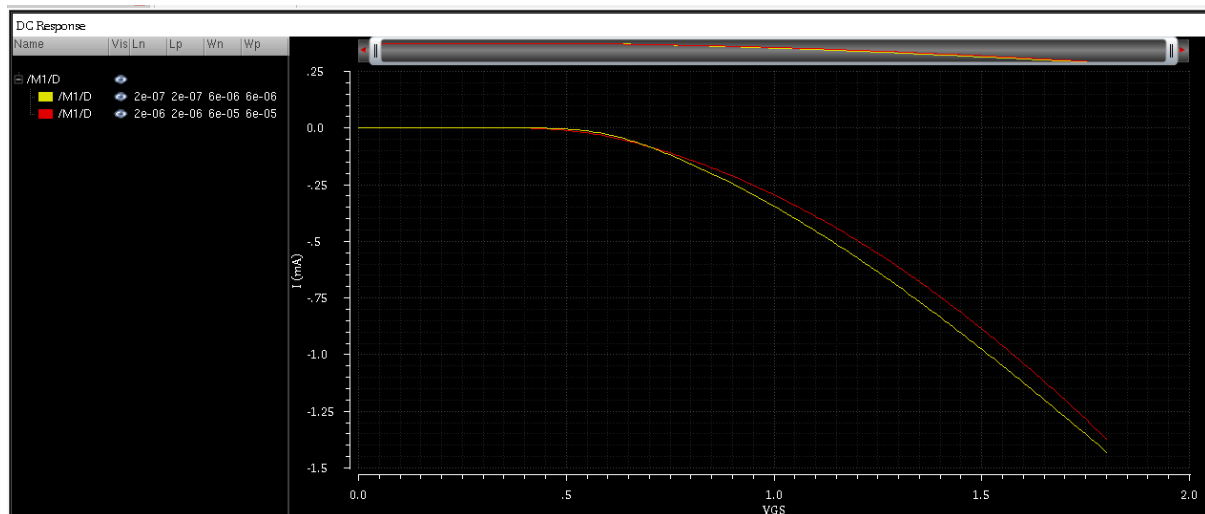PMOS: Long Channel (red) vs Short Channel (yellow)




We can observe that the current is also higher for the long channel device. However, the difference is not as significant as was the case with the NMOS device since the PMOS device is less affected by velocity saturation since its carrier mobility, and therefore its speed, are already relatively low.

So, we conclude that:


- a) Long channel devices have higher currents than short channel devices.
 - b) The relation is quadratic for Long channel devices and almost linear for short channel devices
- 3) Differences between NMOS and PMOS
- a) NMOS has higher current. Due to higher carrier mobility.

b) Ratios are calculated below

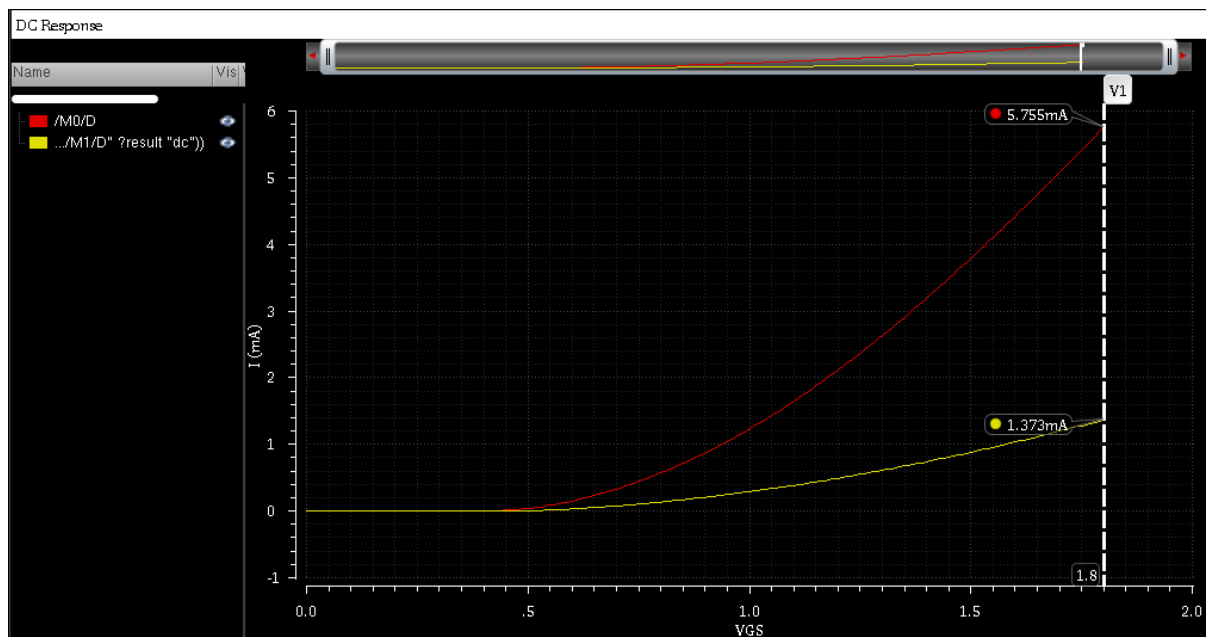

For long channel device, $IDN = 5.755$ mA, and $IDP = 1.373$ mA

so ratio = $5.755/1.373 = 4.19$

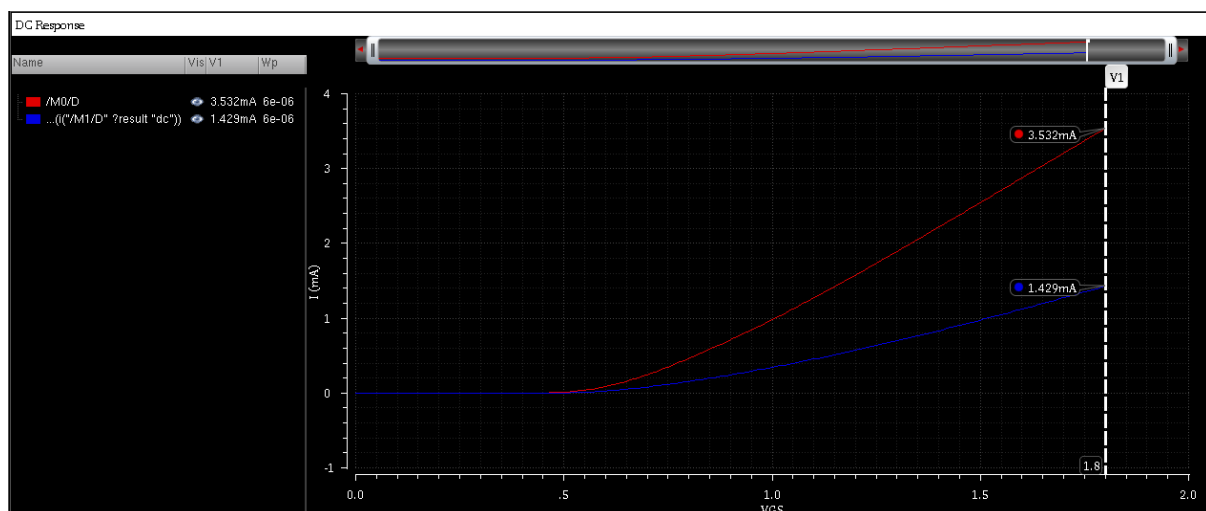

For short channel device, $IDN = 3.532$ mA, and $IDP = 1.429$ mA


so ratio = $3.532/1.429 = 2.47$

c) By comparing ratios and absolute values obtained,

NMOS is more affected by short channel effect due to its high carrier mobility and speed. PMOS already has low carrier mobility and speed so the effect of short channel is not as noticeable as with NMOS.

2. g_m vs V_{GS}

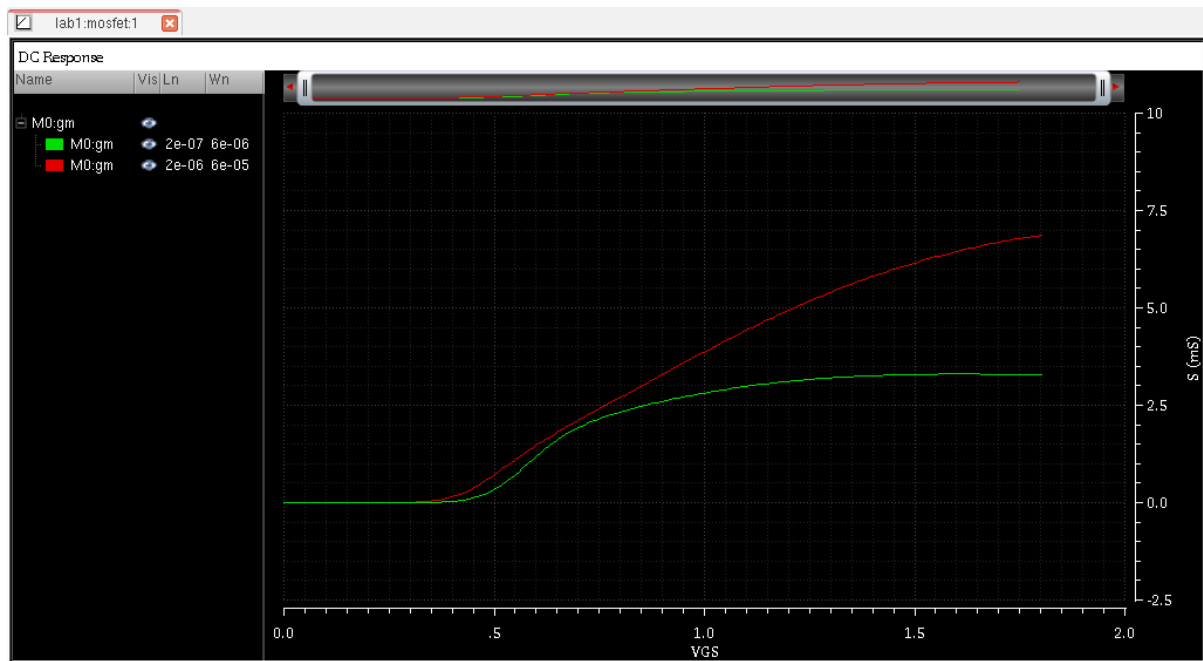1) g_m for short channel (green) and g_m for long channel (red) are shown.




2) g_m doesn't vary linearly with V_{GS} . g_m depends on the Q-point of the device, the device geometry (W/L), and the doping type. All these factors are non-linear and differ in different regions of operations, hence g_m is not linearly related to V_{GS} .

Does g_m saturate?


Yes, g_m saturates. In the triode region, the transconductance g_m is a function of V_{GS} and hence increases with its increase. As V_{GS} gets larger and the MOSFET enters the triode region, I_D saturates, and g_m is no longer a function of V_{GS} , hence it saturates.

3.ID vs VDS

For short channel device

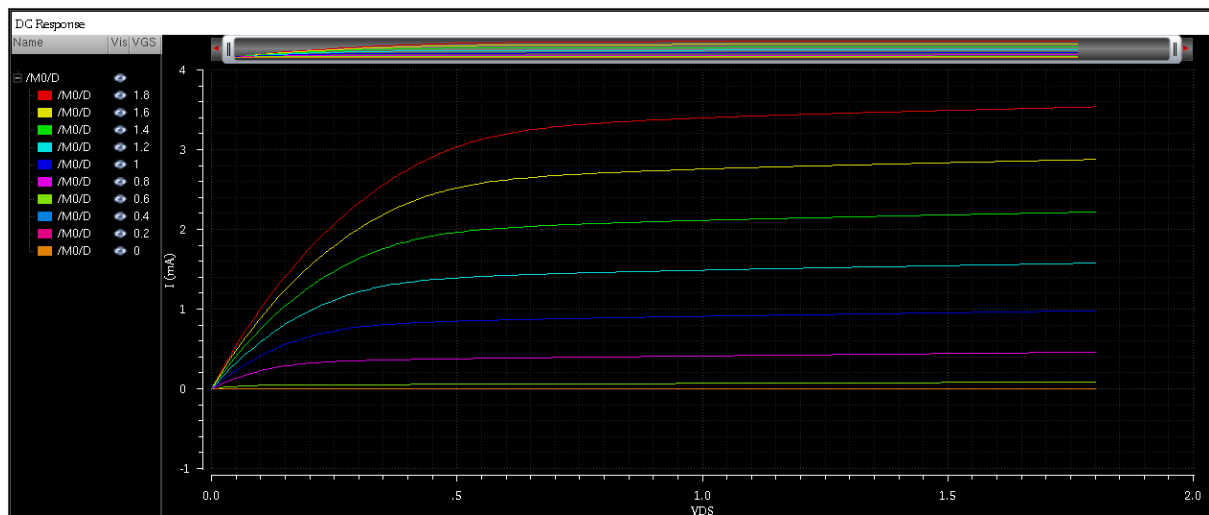

For long channel device

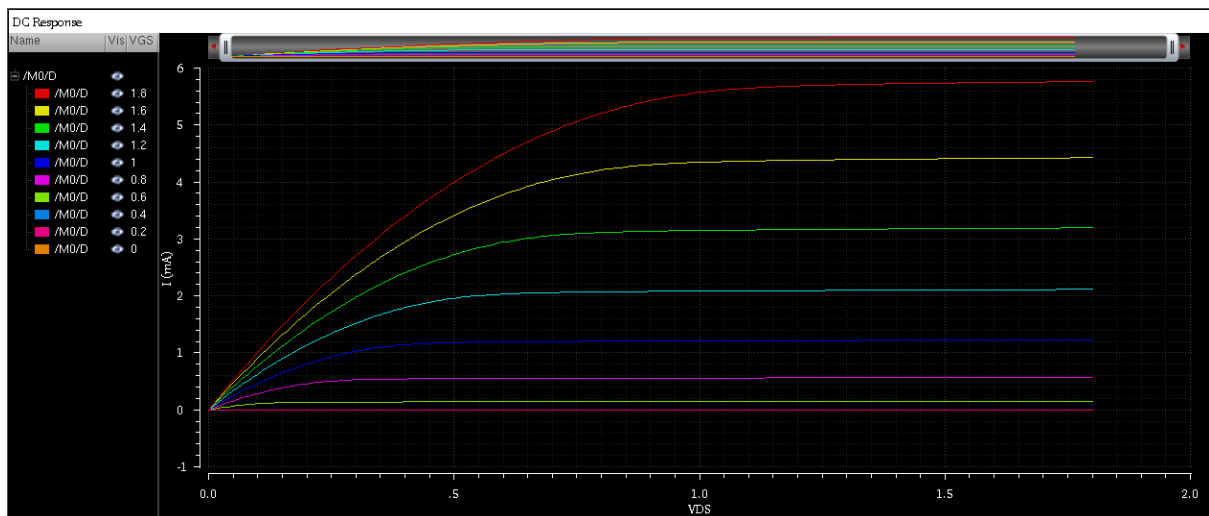


Long channel NMOS has a higher current than the short channel NMOS.

This is because the long-channel device has a longer channel length and a higher resistance, which results in a more gradual increase in the electric field along the channel, giving a steeper slope of the I_D vs V_{DS} curve.

4. *gm and ro in triode and saturation regions*

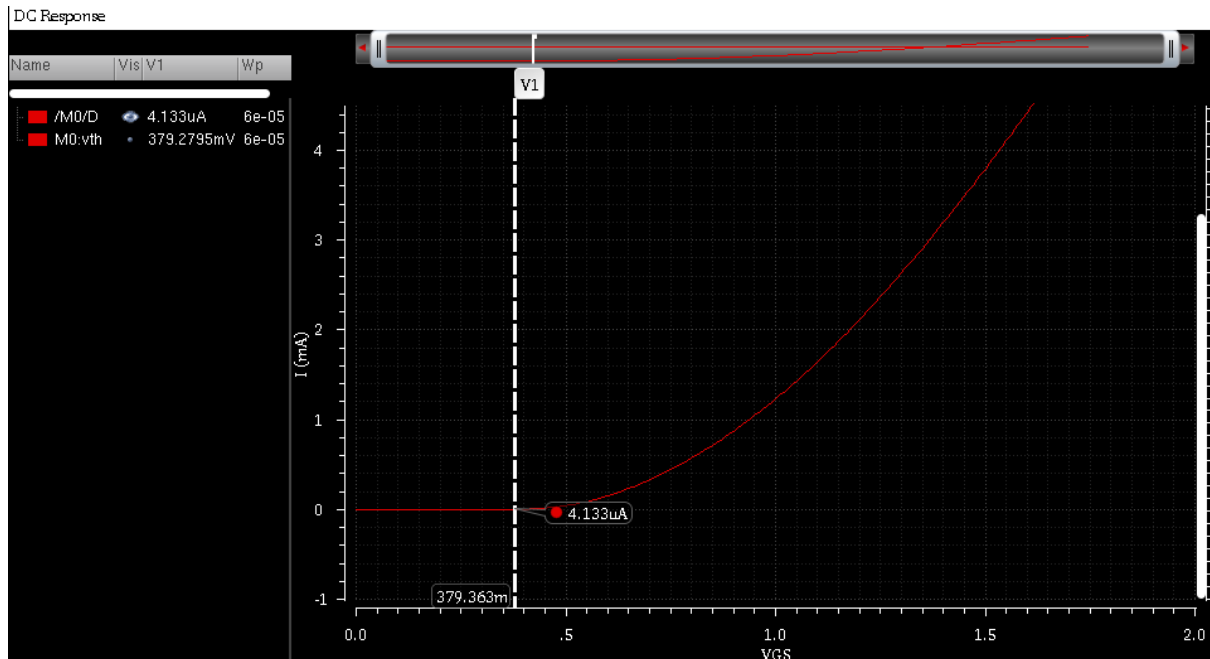
1) First, we will use the graph of I_D vs V_{GS} to obtain an estimate for V_{TH} ; At the point where I_D starts to grow above zero, Transistor enters into the ON region and $V_{GS} = V_{TH}$.




From the graph of I_D vs V_{GS} , $V_{TH} = 0.38$, approximately.

Hence $V_{GS} = V_{TH} + 0.5 = 0.88$.

This is a plot for I_{DS} vs V_{DS}

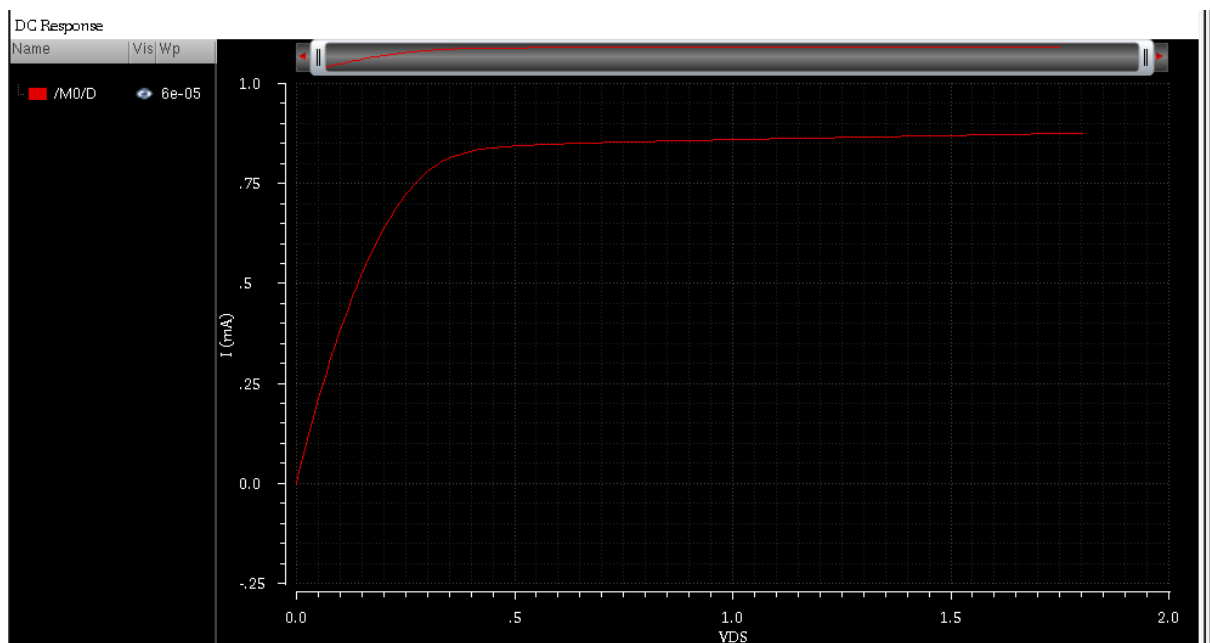


This is the plot of g_m vs V_{DS}

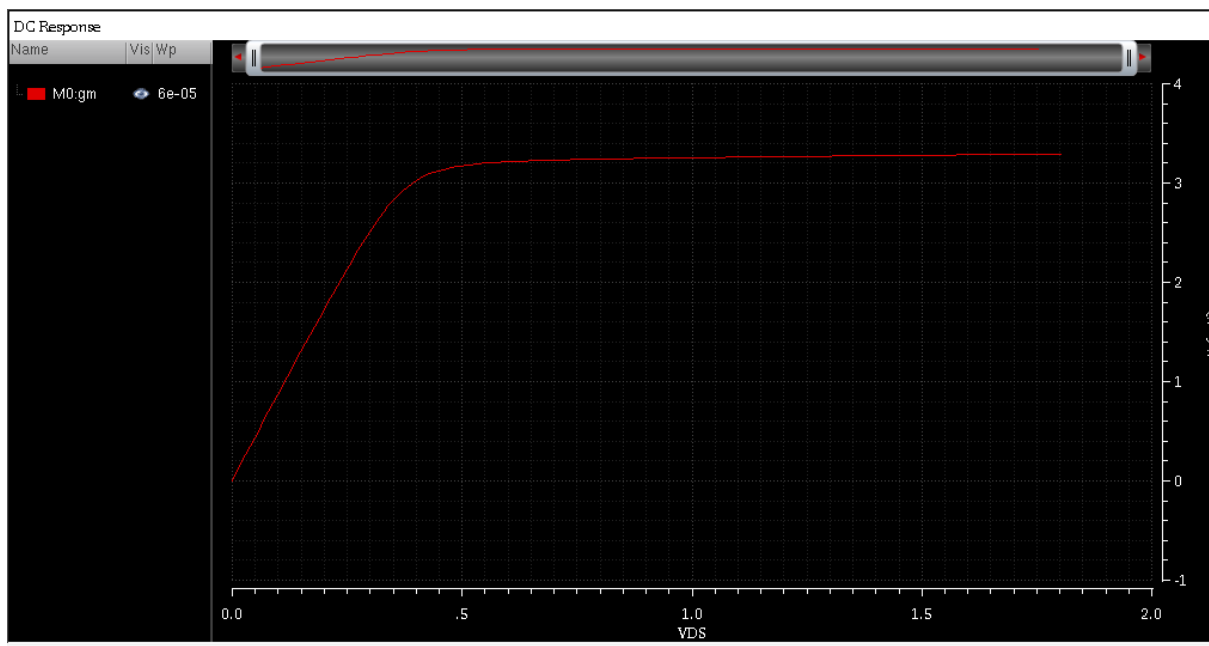

- a) Yes, in the first part of the graph the relation is linear.
- b) Yes, g_m saturates since g_m is proportional to I_D and I_D itself saturates beyond V_{ov} .
- c) For analog amplifier applications, it will be preferred to bias a transistor in the active region especially the saturation region because The biasing point can be chosen to provide a suitable operating point in the saturation region, where the transistor can provide linear amplification of the input signal without distortion or excessive power dissipation.

r_o ($1/g_{ds}$) vs V_{DS}

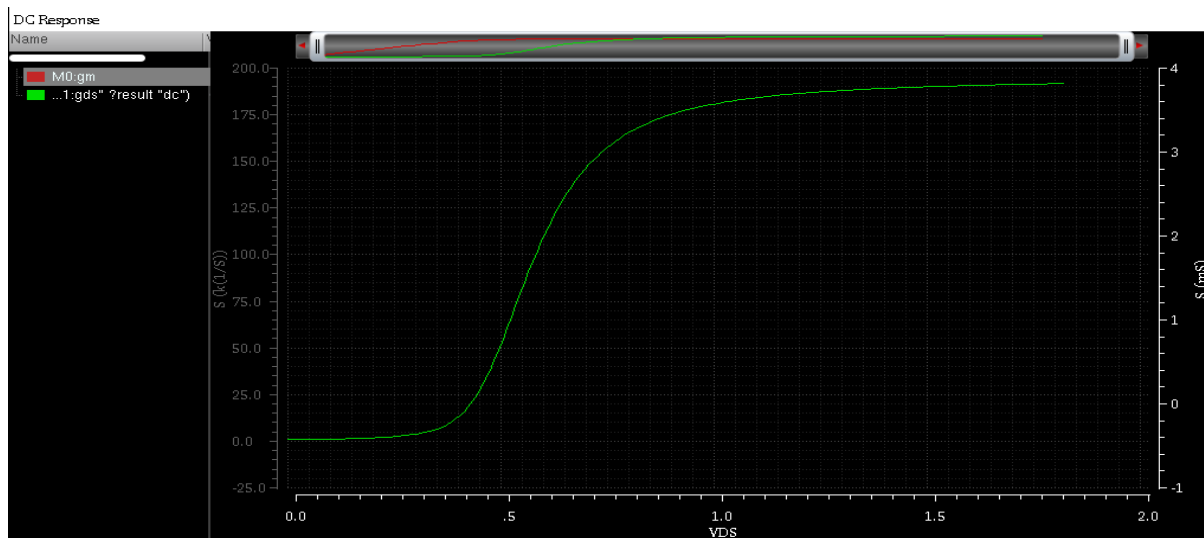

a) No. Since the change in I_D becomes very small, and given that g_{ds} is the rate of change in I_D wrt V_{DS} and since $r_o = 1/g_{ds}$, so r_o increases. If we ignore channel length modulation, change in $I_D = 0$, so $g_{ds} = 0$, and hence r_o should be infinite.

b) since r_o is given by $r_o = 1/(\lambda * I_D)$ and since I_D can still increase in the saturation region, then r_o will decrease. This happens when we take into effect channel length modulation.

c) No. It is recommended to bias the transistor in the saturation region, but not at the edge of saturation. The biasing point should be chosen to provide a suitable operating point in the saturation region, where the transistor can provide linear amplification of the input signal without excessive power dissipation or distortion. The specific choice of biasing point depends on the specific requirements of the amplifier circuit and the characteristics of the NMOS transistor.

d) For analog amplifier applications, it will be preferred to bias a transistor in the active region especially the saturation region because The biasing point can be chosen to provide a suitable operating point in the saturation region, where the transistor can provide linear amplification of the input signal without distortion or excessive power dissipation.